

**Q-1 Select the correct option from the following questions.****10**

- 1 \_\_\_\_\_ is way to simplify the equation.  
A. Boolean Algebra      B. K-MAP      C. BOTH      D. NONE
- 2  $A + A'B + A'B' = ?$   
A. 1      B. 0      C. A      D. A'
- 3 In k-map, octets eliminates \_\_\_\_\_ variable.  
A. one      B. two      C. three      D. four
- 4 The relationship between a function and its binary variables can be represented in \_\_\_\_\_.  
A. truth table      B. decoder      C. encoder      D. multiplexer
- 5 A combinational circuit that performs the arithmetic addition of two bits is called \_\_\_\_\_.  
(A) Full Adder      (B) Half Adder      (C) Binary Adder      (D) Decoder
- 6 A \_\_\_\_\_ is a memory element that stores a binary digit.  
A. binary adder      B. decoder      C. multiplexer      D. flip-flop
- 7 In D flip-flop, when CLK is low then input is \_\_\_\_\_.  
A. high      B. low      C. Don't care      D. Not change
- 8 A multiplexer also called a \_\_\_\_\_.  
A. data multiplier      B. data selector      C. data inverter      D. data remover
- 9 The NOR gate has two or more input signals. If all inputs are \_\_\_\_\_, the output is high.  
A. low      B. high      C. both A and B      D. none
- 10 7. In Comparator, \_\_\_\_\_ gate is use for comparing bits in word.  
A XOR      B AND      C NOR      D XNOR

**Q-2 Answer the following questions. (ATTEMPT ANY TEN)****20**

- 1 Describe the NAND, NOR gate.
- 2 Explain commutative law.
- 3 Draw the circuit for :  $(A \oplus B)'(BC)(A \oplus C)$
- 4 Describe quad in k-map

(P.T.O.)

- 5 Simplify using k-map  $F(A,B,C)=\Sigma(1,2,5)$
- 6 Describe encoder in short.
- 7 Draw the circuit of half adder.
- 8 Describe binary adder in short.
- 9 Define : Flipflop, Register
- 10 Explain D flip-flop in short.
- 11 Define : shift register. What are the types of shift register?
- 12 Draw the circuit of Ring counter.

Q-3 A Write note on: De'Morgan's first and second theorems. 10

OR

Q-3 B Explain AND, XOR, NAND gates. 10

Q-4 A Explain 3x8 line decoder in detail. 5

B What is k-map? Explain octet with example. 5

OR

Q-4 A Explain SOP in detail. 5

B Explain comparator with example. 5

Q-5 A Explain full adder in detail. 4

B Explain 4x1 multiplexer 6

OR

Q-5 A Explain Half adder with an example. 4

B Explain binary subtractor in detail. 6

Q-6 A Explain shift left register. 5

B Explain ring counter in short. 5

OR

Q-6 A Explain shift-right register. 5

B Explain controlled buffer register. 5

—————X—————