

SARDAR PATEL UNIVERSITY**M. Sc. I. T. (Integrated) Examination, 2nd Semester****Wednesday, 13th April, 2016****PS02EIT01: Digital Electronics****Time: 10:30 AM to 12:30 PM****Total Marks: 70**

Note: Answer of all the questions (including Multiple Choice Questions) should be written in the provided answer book only

Q:1 Give answers of following Multiple Choice Questions [10]

- [01] De Morgan's first theorem says that a NOR gate is equivalent to a _____.
(A) bubbled OR (B) bubbled NOR
(C) bubbled AND (D) AND bubbled
- [02] A combinational circuit that performs the arithmetic addition of two bits is called _____.
(A) Full Adder (B) Half Adder
(C) Binary Adder (D) Decoder
- [03] Half adder consists of _____ and _____ Gates
(A) XNOR, AND (B) XNOR, OR
(C) XOR, AND (D) XOR, OR
- [04] A 4 - to - 1 line multiplexer requires _____ data select line.
(A) 1 (B) 2
(C) 3 (D) 4
- [05] Which device has many input and one output?
(A) Flip - Flop (B) Multiplexer
(C) De-Multiplexer (D) Counter
- [06] In Comparator, _____ gate is use for comparing bits in word.
(A) XOR (B) AND
(C) NOR (D) XNOR
- [07] In k-map, quad eliminates _____ variable.
(A) One (B) Two
(C) Three (D) Four
- [08] The 4-variable Karnaugh Map (K-Map) has _____ rows and _____ columns
(A) 2, 2 (B) 4, 4
(C) 4, 2 (D) 2, 4
- [09] Which of the following is Universal flip-flop?
(A) JK flip-flop (B) RS flip-flop
(C) Master slave flip-flop (D) D flip-flop
- [10] Shift register move the stored bits _____ or _____.
(A) Left or right (B) Left or left
(C) Right or right (D) Up or down

Q:2 Answer the following short questions (any Ten)

[20]

- [01] Explain De Morgan first theorem.
- [02] Describe binary adder in short.
- [03] Draw the circuit of encoder.
- [04] Draw the circuit of Seven Segment Decoder.
- [05] Draw the circuit of 4x1 line multiplexer.
- [06] Draw the circuit of 4x1 line de-multiplexer.
- [07] Define Karnaugh map in detail.
- [08] Explain K-Map for 2 variable with example.
- [09] Describe octet in k-map
- [10] Draw circuit diagram of D flip-flop
- [11] Define flip-flop.
- [12] Explain shift left register in brief.

Q:3 [A] Explain half adder in detail.

[05]

[B] Explain 8x3 line encoder in detail.

[05]

OR

Q:3 [C] Explain binary adder-subtractor in detail.

[05]

[D] Explain 3x8 line decoder in detail.

[05]

Q:4 [A] Explain 8x1 line multiplexer with circuit in detail.

[05]

[B] Write a short note on Comparator with circuit diagram.

[05]

OR

Q:4 [C] Explain 8x1 line de-multiplexer with circuit in detail.

[05]

[D] Write a short note on Nibble Multiplexer with circuit.

[05]

Q:5 [A] What is k-map? Explain pair and quad with example.

[05]

[B] Simplify this using k-map $F(A,B,C,D)=\sum(1,3,5,6,8,11,15)$

[05]

OR

Q:5 [C] Write a short note on Don't Care Condition.

[05]

[D] Simplify this using k-map $F(A,B,C,D)=\sum(1,2,5,6,8,12,14)$

[05]

Q:6 [A] Explain RS flip-flop in detail.

[05]

[B] Explain controlled buffer register in detail.

[05]

OR

Q:6 [C] Explain JK flip-flop in detail.

[05]

[D] Explain ring counters in detail.

[05]

— X —
(2)